

**ELEC ENG – 2CJ4**

# **Laboratory Experiments (Set 4)**

**By: Erion Keka, 400435050**

**Professor: Mohamed Elamien**

**03/25/2024**

1.

$$\begin{aligned}
 V_{th1} &= \frac{R_1}{R_1 + R_2} \cdot V_{out+} = \frac{1K\Omega}{(1K\Omega + 22K\Omega)} \cdot 5V = 0.217V \\
 V_{th2} &= \frac{R_1}{R_1 + R_2} \cdot V_{out-} = \frac{1K\Omega}{(1K\Omega + 22K\Omega)} \cdot -5V = -0.217V \\
 T_{TOTAL} &= RC \left( \ln \left( \frac{V_{out+} - V_{th2}}{V_{out+} - V_{th1}} \right) + \ln \left( \frac{V_{out-} - V_{th1}}{V_{out-} - V_{th2}} \right) \right) \\
 &= (100nF \times 50K\Omega) \left[ \ln \left( \frac{5 - (-0.217)}{5 - (0.217)} \right) + \ln \left( \frac{-5 - (0.217)}{-5 - (-0.217)} \right) \right] \\
 &= 8.69 \times 10^{-4} s = 0.869 ms \\
 \text{Frequency} &= \frac{1}{T_{Total}} = \frac{1}{0.869 ms} = \frac{1}{8.69 \times 10^{-4} s} = 1151 Hz
 \end{aligned}$$

2.

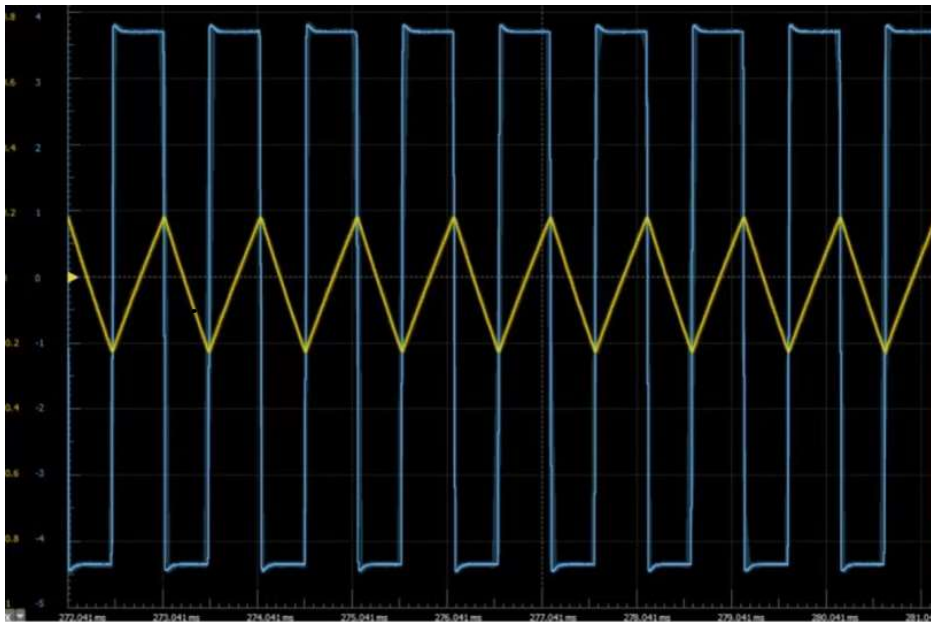


Figure 1: Capacitor Voltage (Yellow Waveform) and Op-Amp Output (Blue Waveform)

From the data, we can notice that the values generated from the Analog Discovery 2 are very similar to those calculated in the theoretical calculations. In the theoretical calculations, a frequency of 1151 Hz was calculated. From the measurements, we obtained roughly a frequency of 1030 Hz. This results in a percent difference of 11.18% which is determined through the formula:  $|V1 - V2| / [(V1 + V2) / 2]$ . The discrepancies that arise may occur due to the usage of a 49.9 Kohm resistor rather than the 50 Kohm resistor and issues with wires.

3. Yes. We can utilize the LM358 Op-Amp to generate a triangular output. In Lab 3, an integrator circuit was utilized to generate a triangular output wave from a square input wave. By feeding the outputted waveform from Lab 4 into the input of the integrator circuit from Lab 3, we will be able to generate a triangular wave output. The graph shown below demonstrates the functionality of Lab 3.

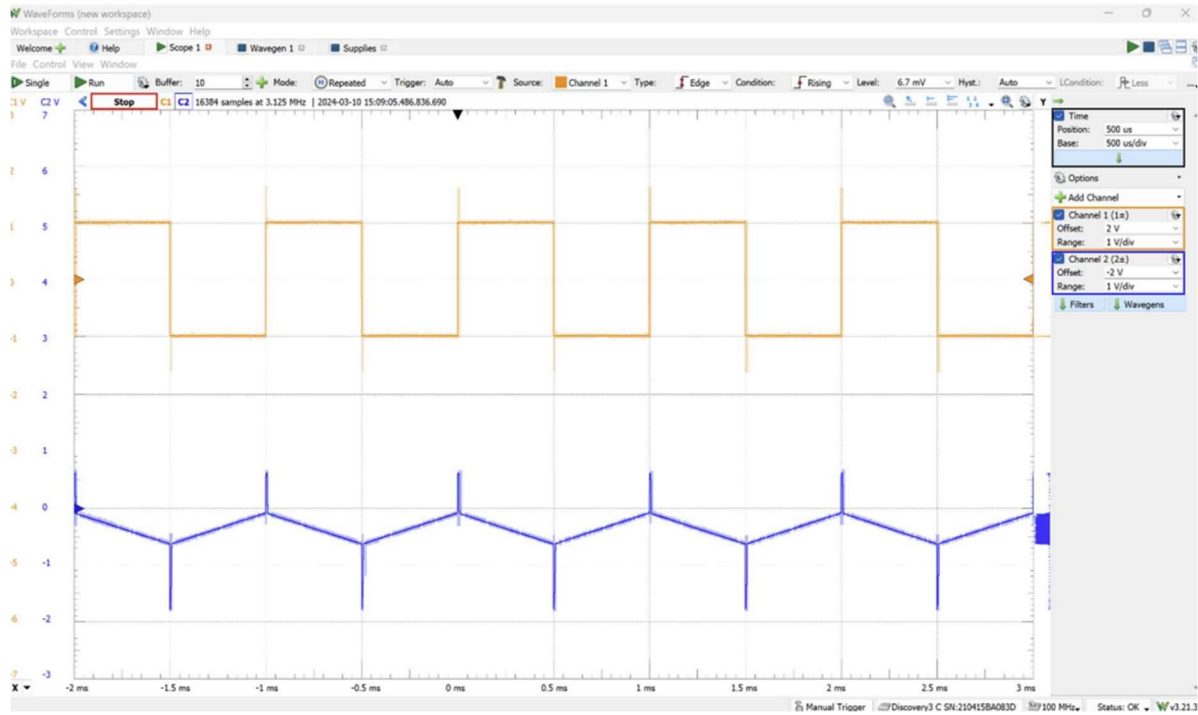


Figure 2: Square Wave Input into Triangular Wave Output