

ELEC ENG – 2CJ4

Laboratory Experiments (Set 2)

By: Erion Keka, 400435050

Professor: Mohamed Elamien

02/25/2024

1. When $V_{in}(t)$ is increased or decreased such that $V_{th2} < V_{in}(t) < V_{th1}$, the output remains the same due to the Schmitt Trigger Circuit. The Schmitt Trigger Circuit takes in a noisy-sinusoidal circuit and converts it into a smooth square-wave function. The voltages that are defined as the threshold voltages, V_{th1} and V_{th2} respectively are the transition voltages that go from low to high, if we were to go below the V_{th2} , a lower output would be desired and the opposite for the V_{th1} . If the input voltage lies within the $V_{th2} < V_{in}(t) < V_{th1}$, the desirable output would be to remain within this threshold.

2.

(V_{ref}, R_1, R_2)	V_{th1} (Theoretical)	V_{th2} (Theoretical)	V_{gap} (Theoretical)
(0V, 4.7k Ω , 4.7k Ω)	2.5V	-2.5V	5V
(0V, 22k Ω , 4.7k Ω)	0.88V	-0.88V	1.76V
(2V, 4.7k Ω , 4.7k Ω)	3.5V	-1.5V	5V
(2V, 22k Ω , 4.7k Ω)	2.53V	0.77V	1.76V

Sample Calculation (1st Row):

given: \downarrow

$V_{out} = \pm 5V$

$$V_{th1} = \frac{R_2}{R_2 + R_1} V_{out+} + \frac{R_1}{R_2 + R_1} V_{ref} = \frac{4.7}{4.7 + 4.7} (5V) + 0 = 2.5V$$


$$V_{th2} = \frac{R_2}{R_2 + R_1} V_{out-} + \frac{R_1}{R_2 + R_1} V_{ref} = \frac{4.7}{4.7 + 4.7} (-5V) + 0 = -2.5V$$

$$V_{gap} = V_{th1} - V_{th2} = 2.5V - (-2.5V) = 5V$$

3.

(V_{ref}, R_1, R_2)	$V_{th1} (Measured)$	$V_{th2} (Measured)$	$V_{gap} (Measured)$
$(0V, 4.7k\Omega, 4.7k\Omega)$	2.232 V	-2.812 V	5.044 V
$(0V, 22k\Omega, 4.7k\Omega)$	1.101 V	-1.01 V	2.111 V
$(2V, 4.7k\Omega, 4.7k\Omega)$	3.069 V	-2.151 V	5.22 V
$(2V, 22k\Omega, 4.7k\Omega)$	2.739 V	0.5213 V	2.2177 V

Circuit Design:

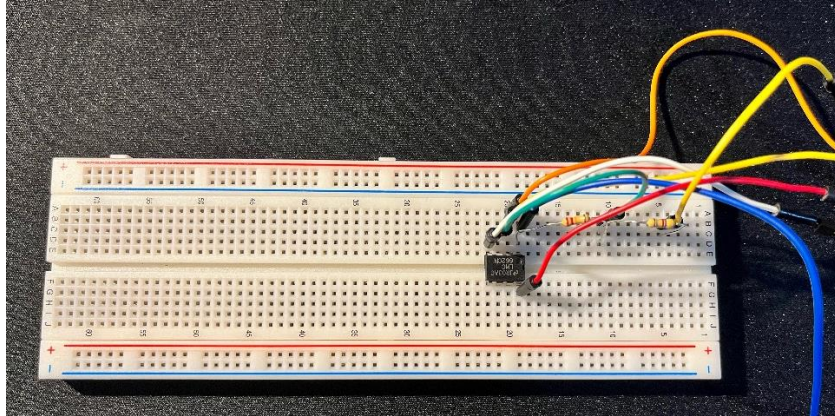


$(0V, 4.7k\Omega, 4.7k\Omega)$:




(2V, 4.7k Ω , 4.7k Ω):



(0V, 22k Ω , 4.7k Ω):

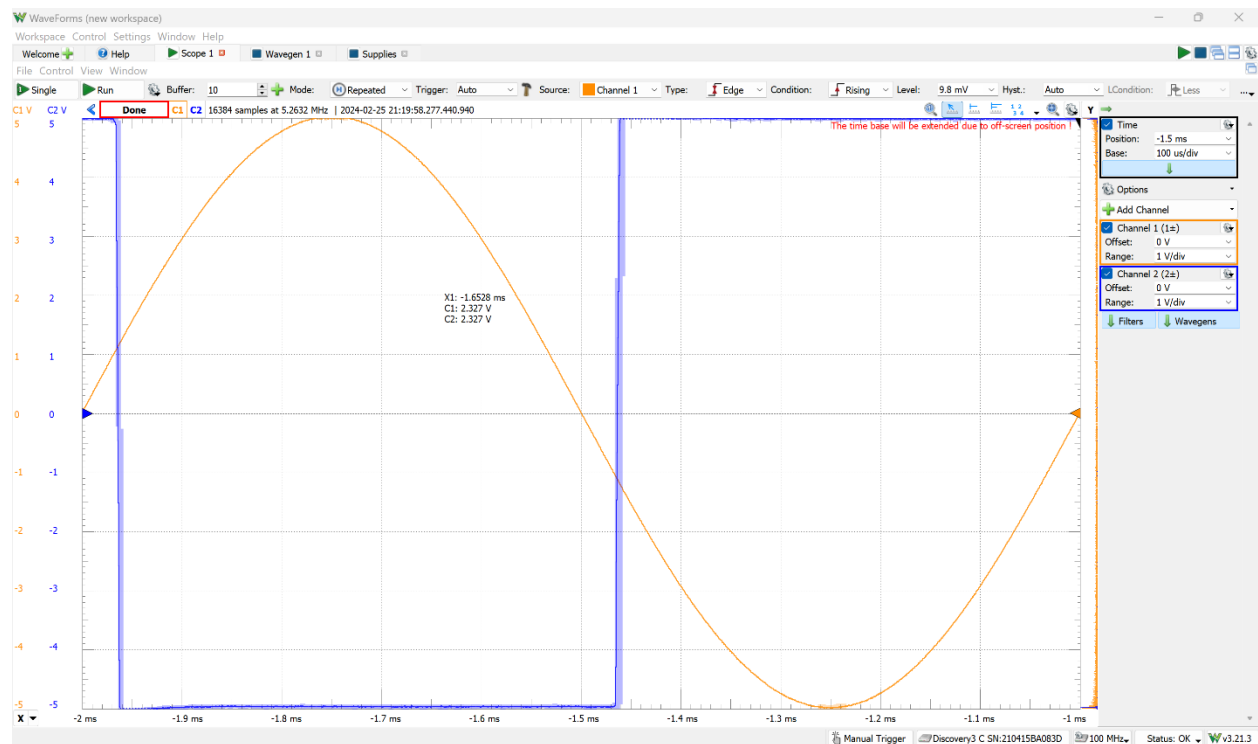

(2V, 22k Ω , 4.7k Ω):

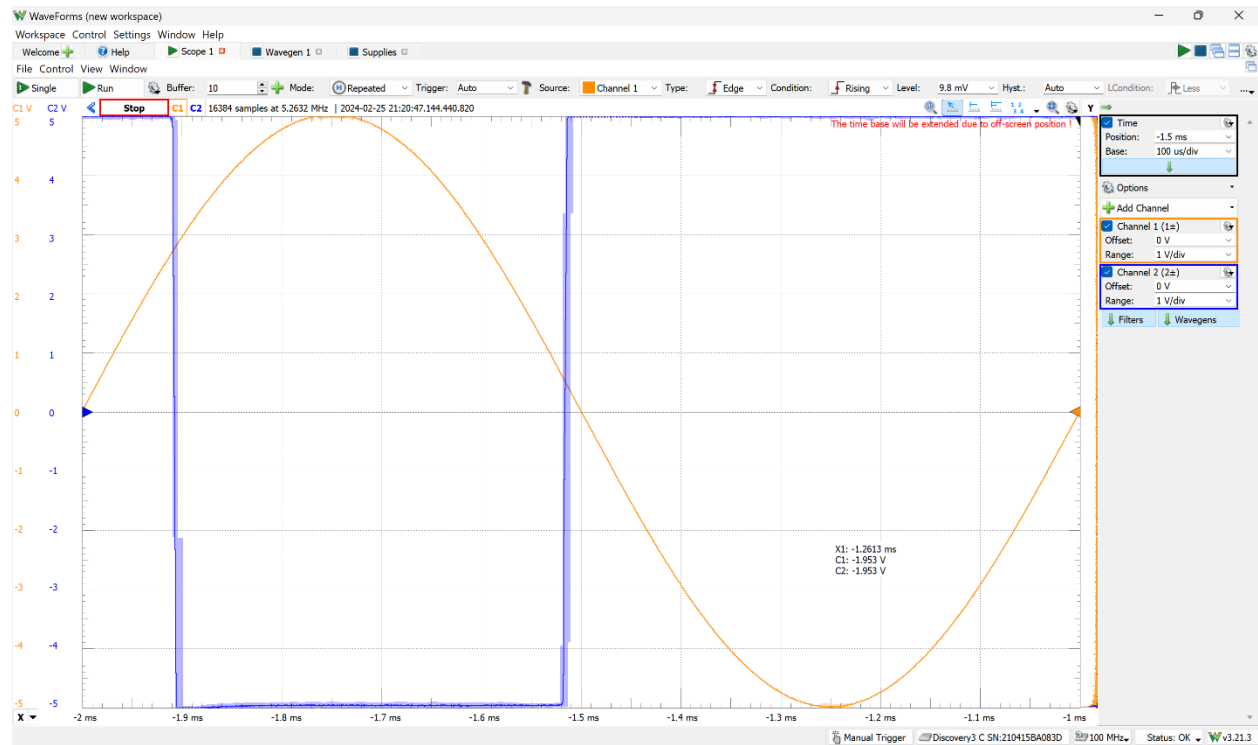

4.

(V_{ref}, R_1, R_2)	V_{th1} (% Difference)	V_{th2} (% Difference)	V_{gap} (% Difference)
(0V, 4.7k Ω , 4.7k Ω)	11.32%	11.747%	0.876%
(0V, 22k Ω , 4.7k Ω)	22.312%	13.756%	18.134%
(2V, 4.7k Ω , 4.7k Ω)	3.609%	35.662%	4.305%
(2V, 22k Ω , 4.7k Ω)	7.933%	38.519%	23.013%

5. V_{gap} is not affected by the change of V_{ref} from zero to a non-zero value. In the theoretical calculations, changing V_{ref} whilst keeping all else the same does not have an impact in V_{gap} . The change in V_{ref} simply results in a shift either upwards or downwards by the value of the reference voltage.